

CARP Meeting


2

MULTIPLIER/DIVIDER

RV32I → RV32IM


Ideal Register / Flip Flop

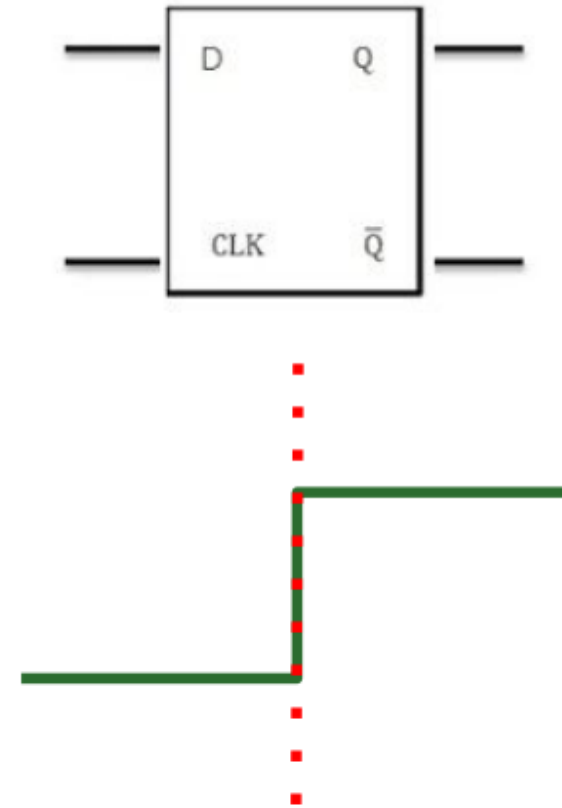- Samples Data perfectly on clock edge
 - Instantaneous Capture on Perfect Edge
- Immune to noise before and after edge
- Always holds a known binary value
 - 0 or 1
- Data is instantly made available to output



Real Register Part 1

 
- Takes some time to sample data
- Requires data to be stable during that time
 - **Setup Time**: min time before the edge that data must remain stable
 - **Hold Time**: min time after the edge that data must remain stable



Glossary


Setup Time t_s : data must be stable t_s before edge

 Hold Time t_H : data must be stable t_H after edge




Real Register Part 2

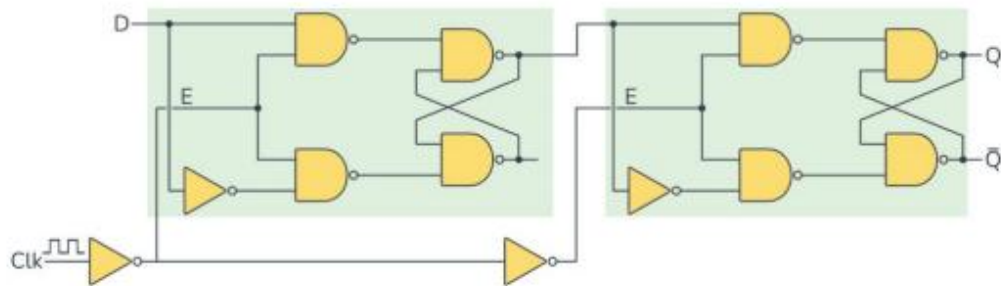- If signal is not stable, risk **metastability**
 - Register will risk incorrect data, or even worse get stuck
- Once sampled, takes some time to propagate to the output
 - t_{co} : clock-to-Q propagation delay



Glossary


 
Metastability: register gets stuck between 0 and 1 states for unknown amount of time



Max Path: Setup Time Violations



- Max Path asks the question:
 - Is your critical path logic too slow to keep up with your clock?
- **Setup Time Violation:** logic is too slow such that data changes past setup time period
 - Fixable by lowering clock frequency
 - Or use faster logic
- Usable Portion of Clock Period:
 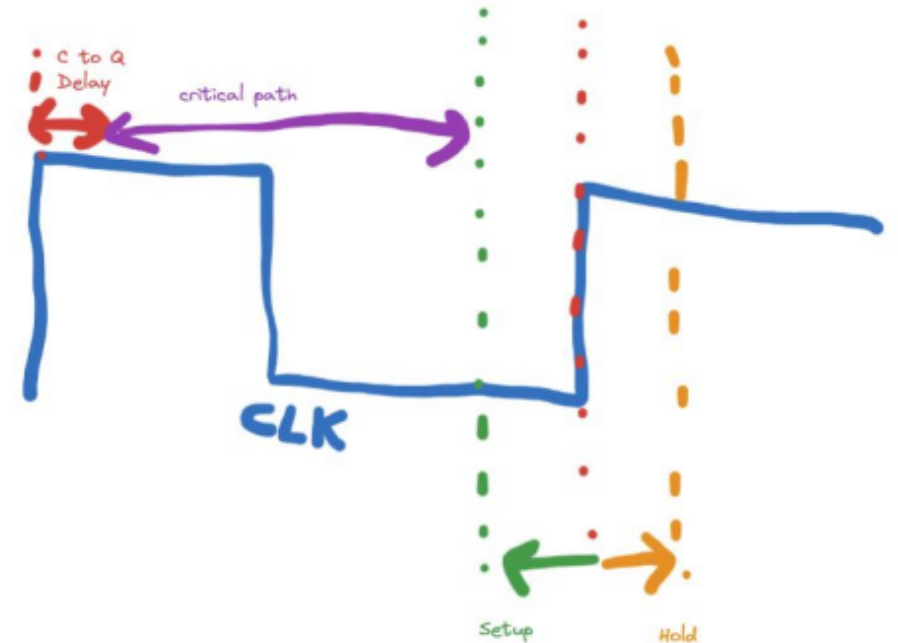
$$t_{\text{logic}} \leq t_{\text{clock}} - t_{\text{setup}} - t_{\text{cq}}$$



Min Path: Hold Time Violations

  - Min Path asks the question:
 - Is your minimum logic path so fast that one register's output will change before the next one has completed hold time?
- **Hold Time Violation:** input to register will change before register is done with its hold time
- Not affected by Clock Speed, only by design
 - **NOT FIXABLE AFTER TAPEOUT**
 - Have to tell the tools (Openlane) to try harder to fix



Slack




- **Slack** is the amount of leeway between your design's timing and a design constraint
- **Max Path:**
 - **Positive Slack** means you are passing your timing requirement.
 - With a positive slack of 3, you could speed up your clock frequency by up to 3
 - **Zero Slack** means you are passing but with no wiggle room
 - **Negative Slack** means you are violating setup time.
 - To fix, slow down your clock frequency by the amount of negative slack
- **Min Path** is not affected by clock frequency
 - **Negative Slack** in your min path is a hold time violation, which the tools will need to fix by inserting dummy logic
- Computing: $\text{Slack} = \text{Required Time} - \text{Arrival Time}$
 - $S = R - A$

STA Example

Delays:

- Buffer: 1
- NAND: 1
- 3-Input NAND: 2
- OR: 2

Clock Period: 5

 

HARDWARE PERFORMANCE TRADEOFFS FOR DUMMIES

COMBINATIONAL = MORE HARDWARE (do everything at once)

- Critical Path = longest logic chain between registers
- Setup Time = time to get through all the logic to the register
- Hold Time = time to hold the data while register captures it

SEQUENTIAL = LESS HARDWARE (do everything in steps, reuse hardware)

- IPC goes way down depending on # of cycles wasted in calculation
- Sometimes worth the cost if hardware too complex

REMEMBER: Critical Path determines CLK frequency

LETS BUILD HARDWARE LIKE A 3rd GRADER!

How does a child
multiply two
numbers?



REPEATED
ADDITION

How does a child
divide two
numbers?



REPEATED
SUBTRACTION

BINARY MULTIPLICATION:

Algorithm: SHIFT-ADD

$$\begin{array}{r} 01001 \text{ (9)} \\ \times 011 \text{ (3)} \\ \hline \end{array}$$

BINARY DIVISION

01001 / (9)
011 (3)

How to handle SIGNED

STEPS

1. CONVERT SIGNED INPUTS TO UNSIGNED (take absolute value)
2. MULTIPLY/DIVIDE UNSIGNED
3. NEGATE THE RESULT AT THE END


How to avoid the extremes

A combinational multiply and divide is a lot of hardware cost, especially when we're considering a hardware limited ASIC implementation for our design.

Let's get the best of both worlds

- Perform multiplication in steps
- Perform each step combinationaly

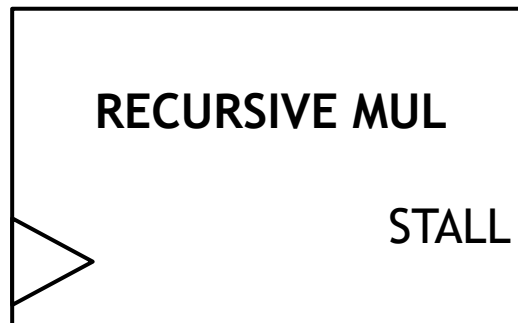INSTEAD OF a big combinational multiplier, or a recursive multiplier with a stall..



PIPELINE!!!!

DO A COMBINATIONAL MULTIPLY ACROSS 3 STAGES!!

31 possible shifts, 32 possible adds

32 bits handled across 3 stages = 10.67 shift-adds per stage (11)

Results in best performance vs logic depth

